



北京交通大学



# Experiment 1

## Full-Adder (全加器)

BJTU

<http://www.dsvlab.cn/>

[https://mp.weixin.qq.com/s/Hhn0dJ\\_D1AcEB-6zcQyXVw](https://mp.weixin.qq.com/s/Hhn0dJ_D1AcEB-6zcQyXVw)



# Contents


- Coding and circuitry - signal conversion
- Gate circuit - Signal correlation
- Adder - Signal calculation
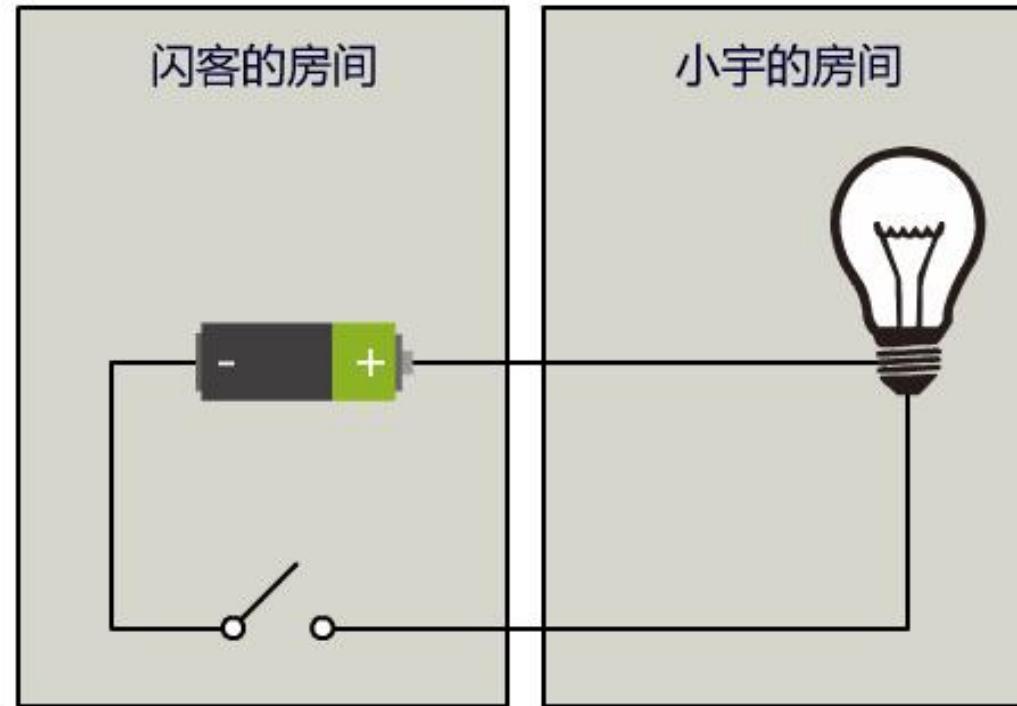
# Coding and circuitry



北京交通大学

Suppose Shanke want to send signal to Xiaoyu:



# Coding and circuitry



北京交通大学

We use the combination of light bulbs to express all the words, and made an agreement to read the state of the light bulbs every second and record it, which is our code.

*I: ON ON OFF OFF ON*

*Like: OFF ON ON OFF OFF*


*You: ON OFF ON OFF ON*

# Gate circuit



北京交通大学

Make the code with two inputs

 

In this way, there is no longer a simple correspondence between the two switches and the bulb, but a **logic**.

# Gate circuit



北京交通大学

The disconnection and connection of the switch correspond to the disconnection and connection of the circuit respectively. The bulb is ON or OFF, also correspond to the circuit's condition. Then the two can be unified.





The connection and disconnection of the switch is active. The ON and OFF of the small bulb, is passive, is the result.
  
# Gate circuit



北京交通大学

We call the connection and disconnection of the switch as the input, and the connection and disconnection of the bulb as the output, and encapsulate the whole circuit in a graph:












We decide to call this circuit a gate circuit(门电路), and the top one is called an **AND** gate.

# Gate circuit



For more abstract exploration in the future, we will represent the circuit connection as the number 1 and the circuit disconnection as the number 0. We call this representation as **binary**.

	Input 1	Input 2	Output	
	0	0	0	
	0	1	0	
	1	0	0	
	1	1	1	

 




# Gate circuit




北京交通大学


and MORE

 


OR gate

 

XOR

 

NOR

 

# Adder - Signal calculation



北京交通大学

Let's start by adding the simplest bits of binary:

$$0+0=0; \quad 0+1=1; \quad 1+0=1; \\ 1+1=10$$


The output can be reformed into

Addend A	Addend B	Sum bit	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
 
# Adder - Signal calculation



The circuit can be composed of XOR gate and AND gate.



Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	0

Input 1	Input 2	Output
0	0	0
0	1	0
1	0	0
1	1	1

# Adder - Signal calculation



This device implements one bit addition in binary, but it is not perfect because it considers only the carry and output of the **two digits**, but not the carry of the **previous digits**, so it is only called a half adder (半加器).




# Adder -

If the previous adders are n



f more

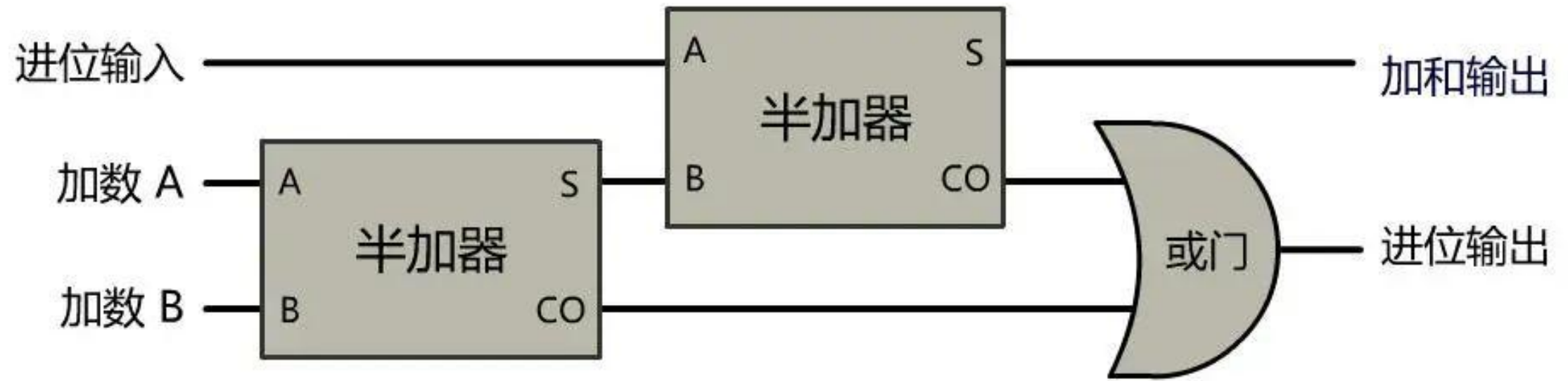



At this point, we have built a perfect one-bit adder, which we call it a full adder.

# Adder - Signal calculation



北京交通大学

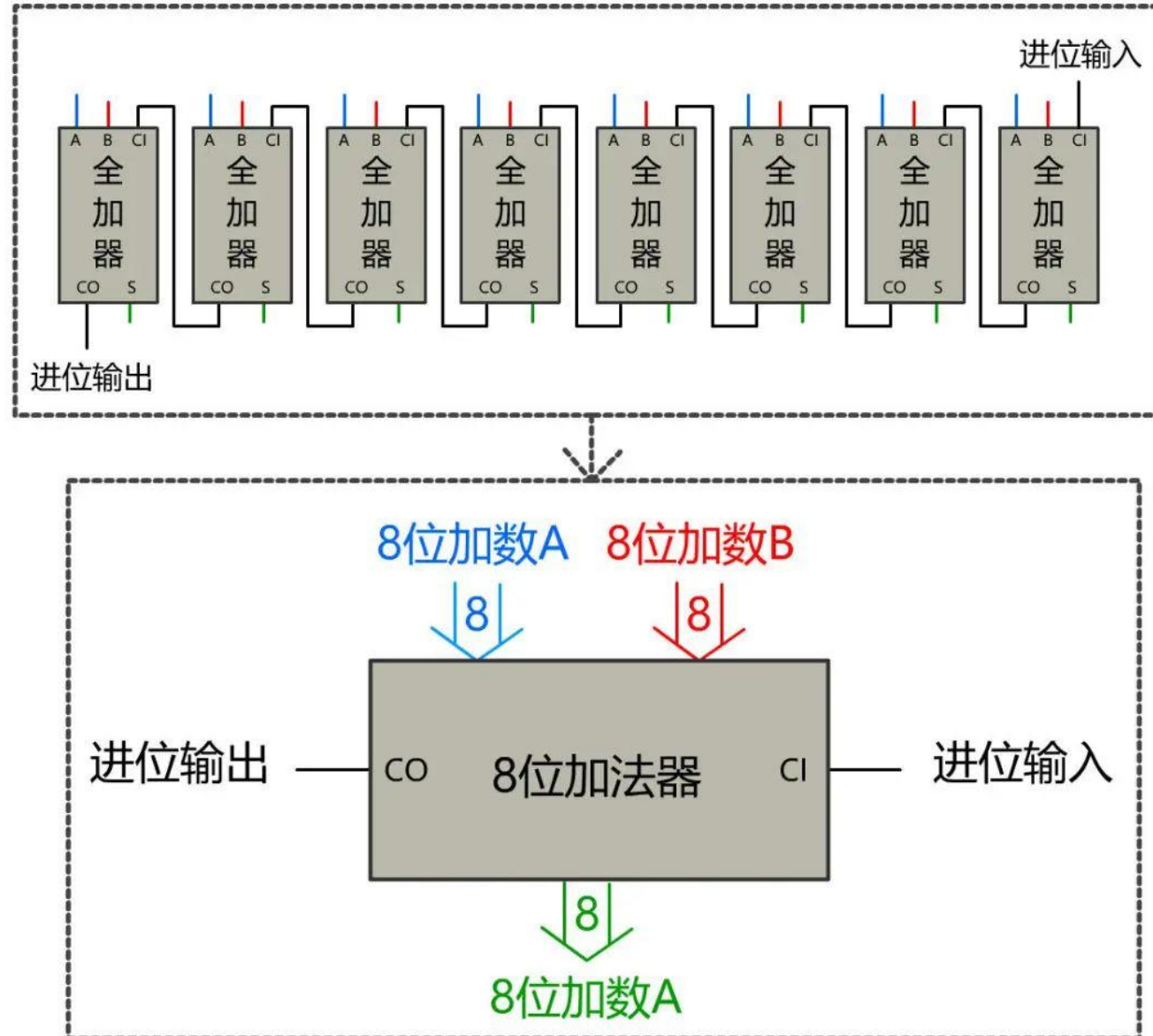


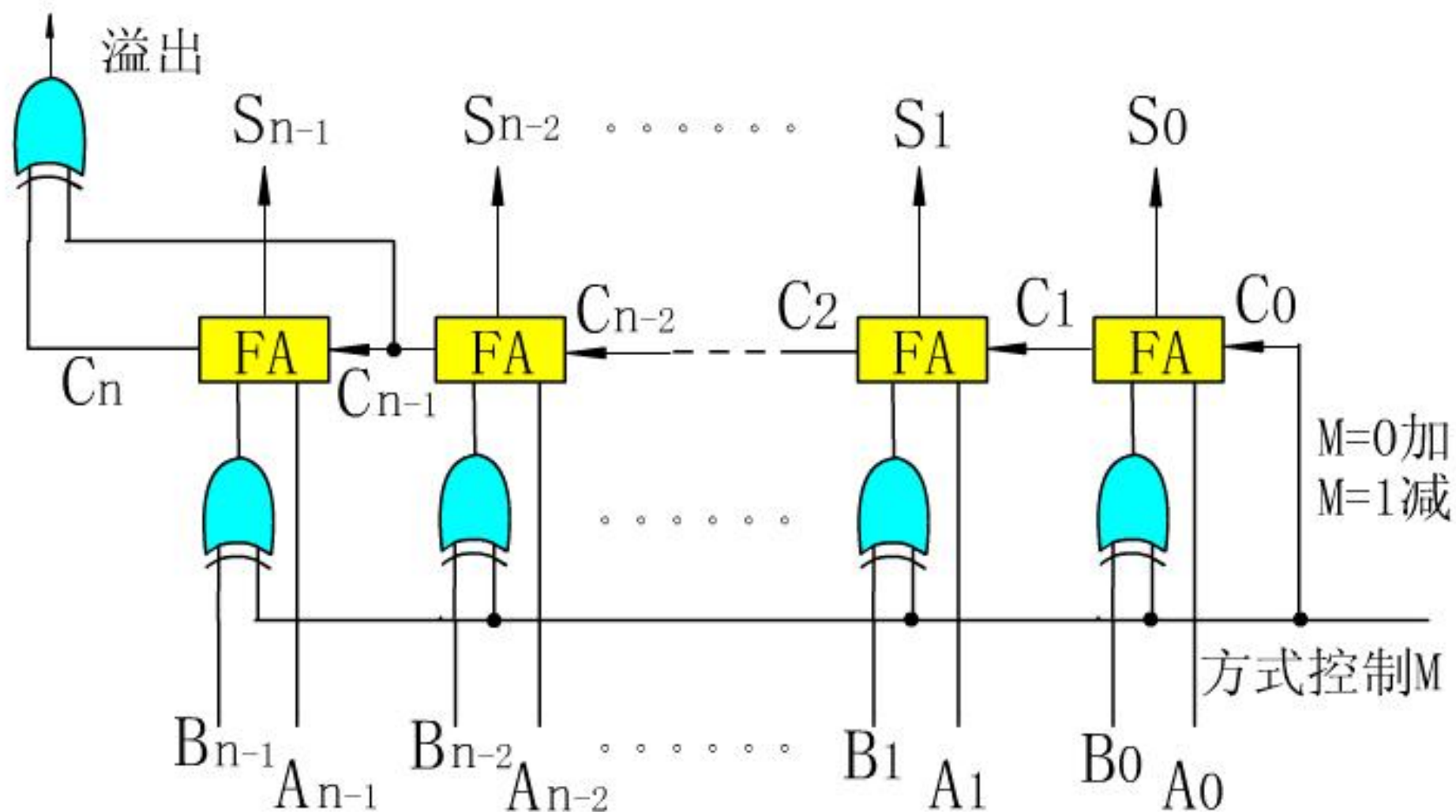

符号位



1010求补后为0110

 




# Half adder




北京交通大学

 

# Full adder




北京交通大学

 

# Two digits adder




北京交通大学

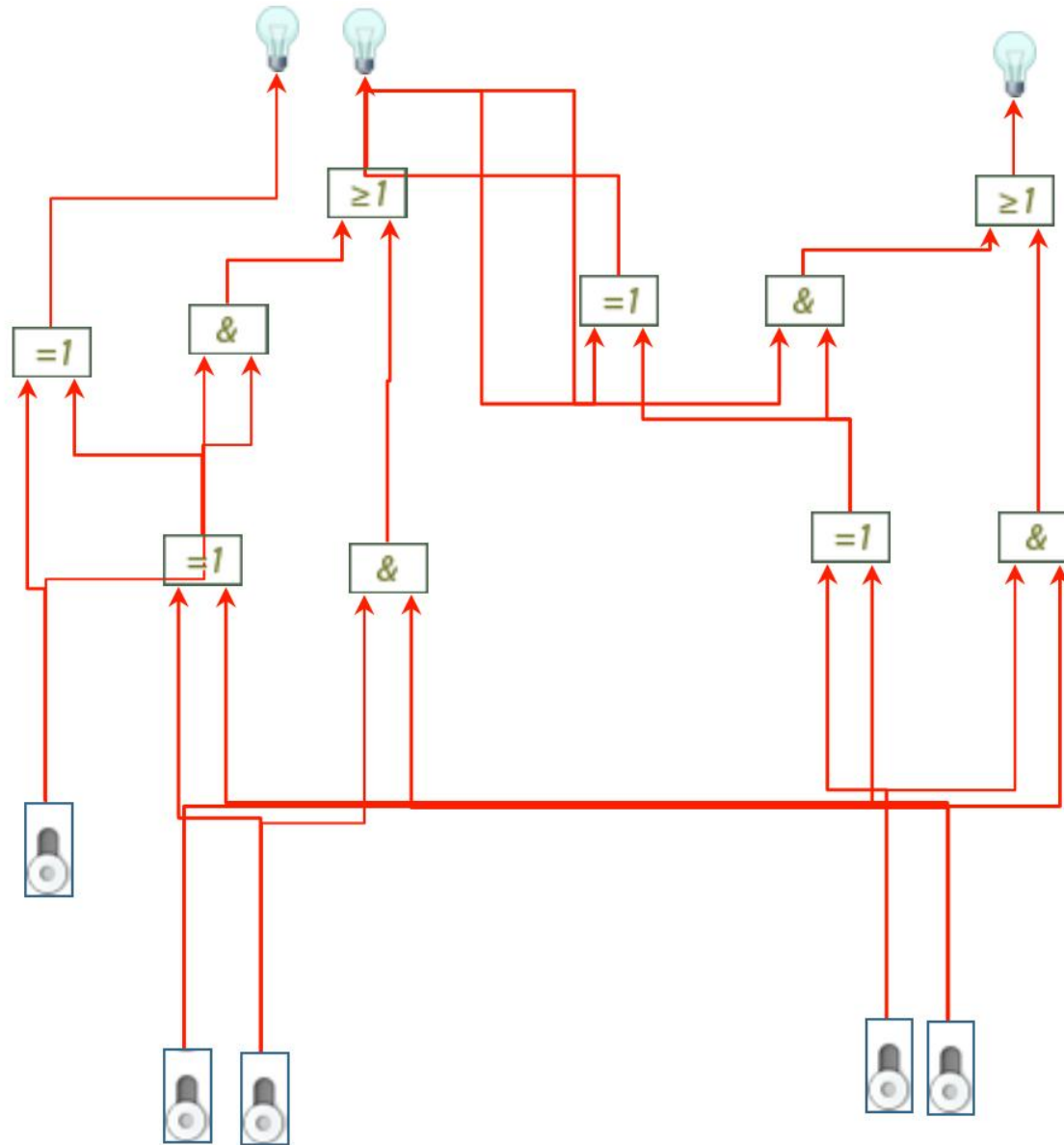

# Three digits adder






北京交通大学

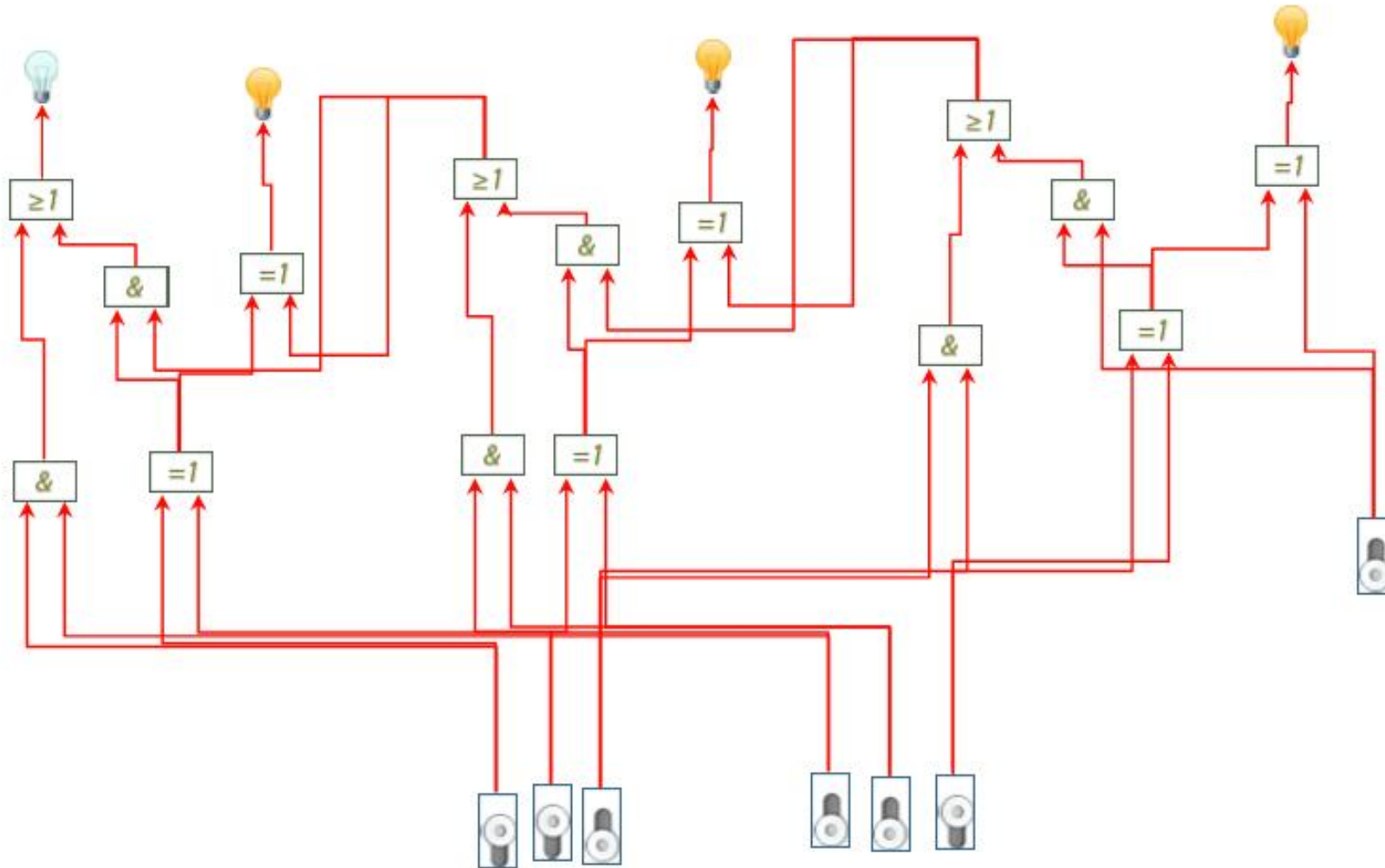

# 2's complement




北京交通大学

  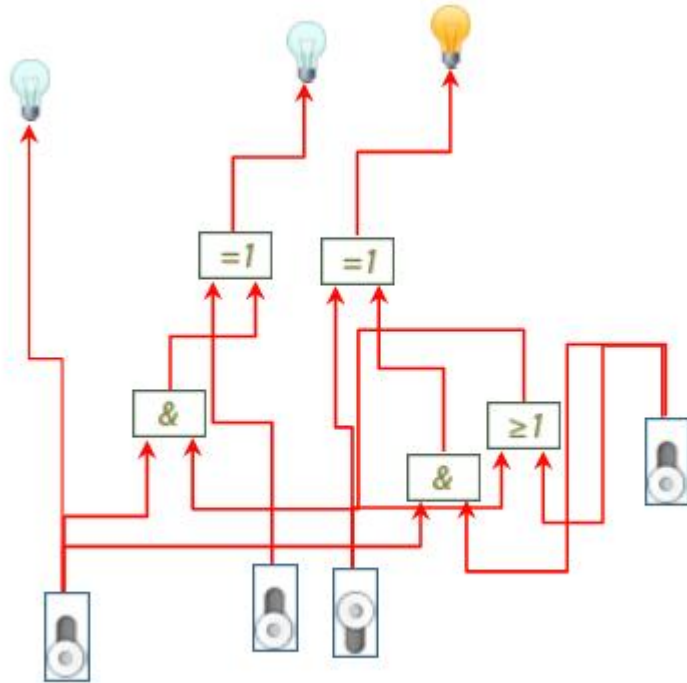

# Adder – 2's Complement with overflow judgment




北京交通大学

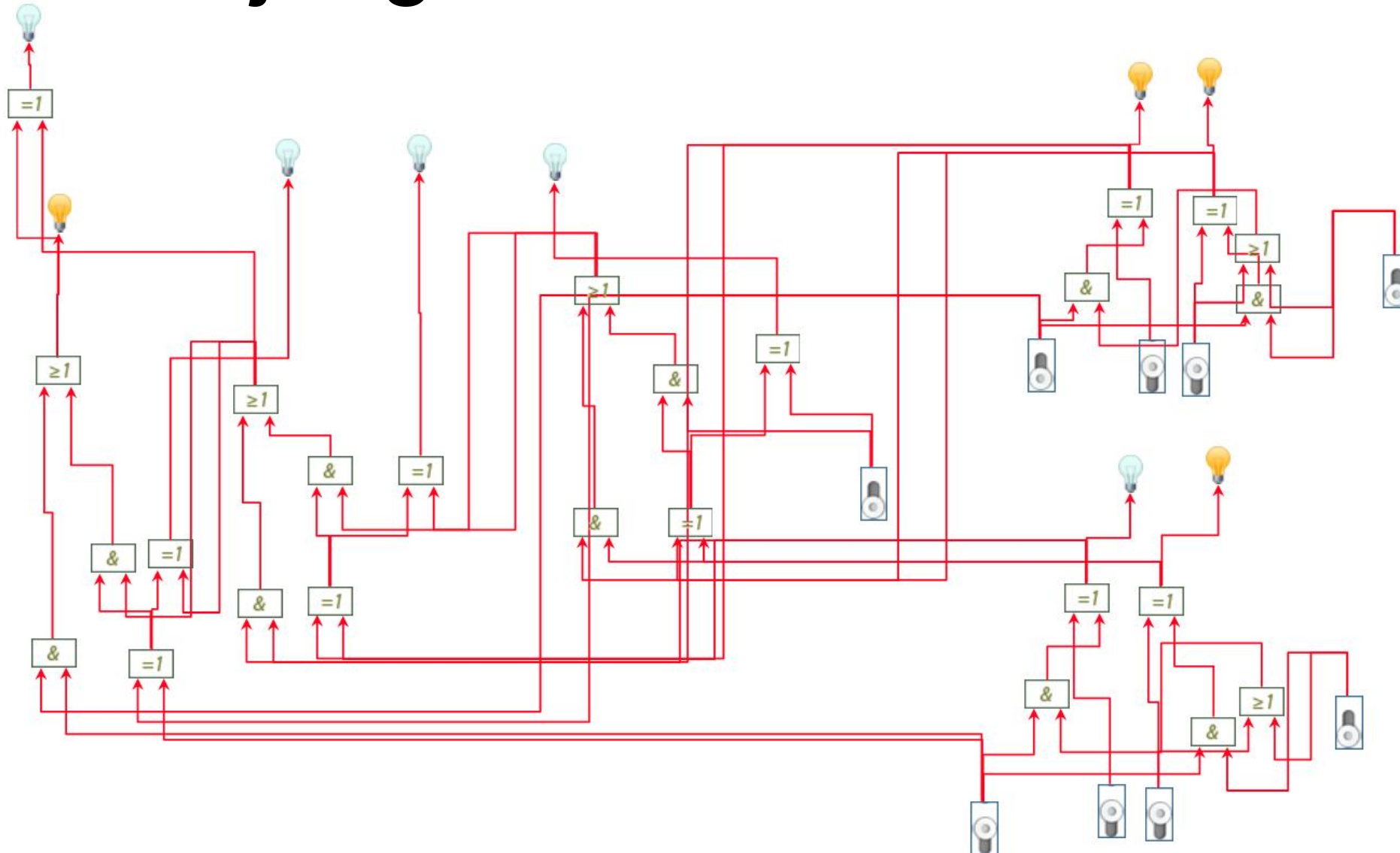

# Adder – convert 2's into TF



北京交通大学

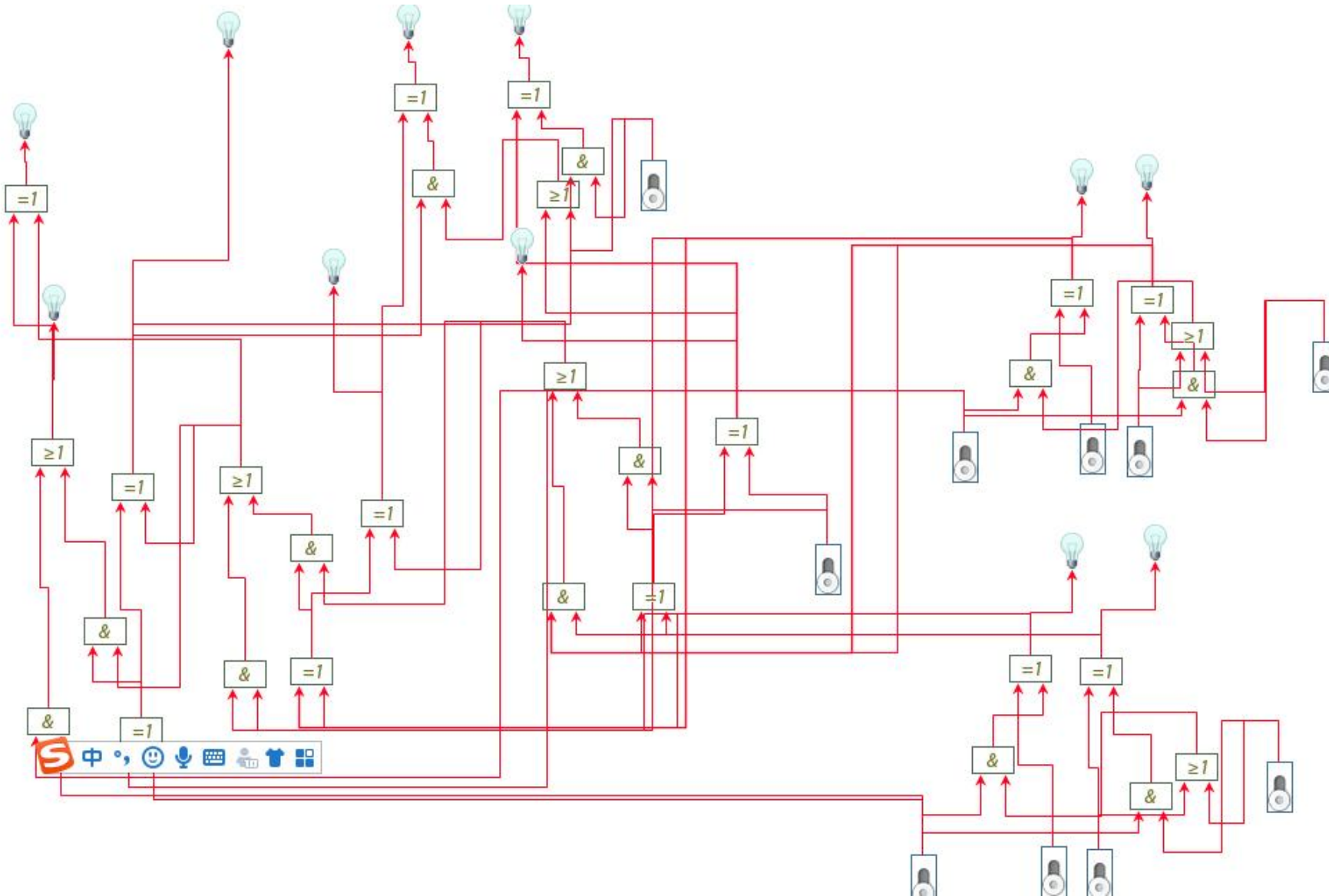



# 实验报告

包括：实验目的、实验原理、实验电路、实验步骤、  
思考与分析（使用**3**位全加器构造出补码加法/减法。  
输入为原码，转换为补码进行运算后再转回原码，  
具有**1**位溢出判断位）